

Meng Wai Chan  
May 13, 2023

## **Final Project**

Meng Wai Chan

Professor Gertner

CSc 343

May 13, 2023

## Tables of Content

<b>I. Objective.....</b>	<b>3</b>
<b>II. Description of Specifications and Functionality.....</b>	<b>3</b>
LPM SRAM of 16 words 32 bits.....	3
LPM AddSub 32 bits.....	4
Demux 1 to 2.....	7
Test Bench.....	8
Addition of Two Integers $X1 + X2$ VHDL.....	10
Subtraction of Two Integers $X1 - X2$ VHDL.....	11
Cumulative Sum $X1 + X2 + X3 + X4$ VHDL.....	12
Cumulative Subtract $X1 - X2 - X3 - X4$ VHDL.....	13
Overflow VHDL.....	14
<b>III. Simulation.....</b>	<b>14</b>
Addition of Two Integers $X1 + X2$ .....	14
Subtraction of Two Integers $X1 - X2$ .....	15
Cumulative Sum $X1 + X2 + X3 + X4$ .....	15
Cumulative Subtract $X1 - X2 - X3 - X4$ .....	16
Overflow.....	17
<b>IV. Conclusion.....</b>	<b>17</b>

## I. Objective

The objective of this final test project is to evaluate our ability to use LPM modules generated from Quartus to design and simulate digital computational circuits. The tasks consist of creating a Static Random-Access Memory (SRAM) using LPM with 16 words and 32 bits. Create a Add/Sub digital circuit using LPM to handle 32 bit addition and subtraction using data from a Memory Initialization File (MIF) to execute and test if our circuit is functioning.

## II. Description of Specifications and Functionality

### LPM SRAM of 16 words 32 bits

```

37 LIBRARY ieee;
38 USE ieee.std_logic_1164.all;
39 LIBRARY altera_mf;
40 USE altera_mf.altera_mf_components.all;
41
42 ENTITY sram IS
43   PORT
44   (
45     address    : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
46     clock      : IN STD_LOGIC := '1';
47     data       : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
48     wren       : IN STD_LOGIC;
49     q          : OUT STD_LOGIC_VECTOR (31 DOWNTO 0)
50   );
51 END sram;
52
53 ARCHITECTURE SYN OF sram IS
54   SIGNAL sub_wire0 : STD_LOGIC_VECTOR (31 DOWNTO 0);
55
56 BEGIN
57   q <= sub_wire0(31 DOWNTO 0);
58
59   altsyncram_component : altsyncram
60     GENERIC MAP (
61       clock_enable_input_a => "BYPASS",
62       clock_enable_output_a => "BYPASS",
63       init_file => "ram_content.mif",
64       intended_device_family => "Cyclone V",
65       lpm_hint => "ENABLE_RUNTIME_MOD=NO",
66       lpm_type => "altsyncram",
67       numwords_a => 16,
68       operation_mode => "SINGLE_PORT",
69       outdata_aclr_a => "NONE",
70       outdata_reg_a => "CLOCK0",
71       power_up_uninitialized => "FALSE",
72       read_during_write_mode_port_a => "NEW_DATA_NO_NBE_READ",
73       widthad_a => 4,
74       width_a => 32,
75       width_byteena_a => 1
76     )
77     PORT MAP (
78       address_a => address,
79       clock0 => clock,
80       data_a => data,
81       wren_a => wren,
82       q_a => sub_wire0
83     );
84 END SYN;

```

Figure 1: SRAM of 16 words 32 bits

```
DEPTH = 16; -- The size of memory in words
WIDTH = 32; -- The size of data in bits
ADDRESS_RADIX = HEX; -- The radix for address values
DATA_RADIX = BIN; -- The radix for data values
CONTENT -- start of (address : data pairs)
BEGIN

00 : 00000000000000000000000000000000; -- memory address : data
01 : 00000000000000000000000000000001;
02 : 00000000000000000000000000000010;
03 : 00000000000000000000000000000011;
04 : 00000000000000000000000000000100;
05 : 00000000000000000000000000000101;
06 : 00000000000000000000000000000110;
07 : 00000000000000000000000000000111;
08 : 00000000000000000000000000001000;
09 : 00000000000000000000000000001001;
0A : 00000000000000000000000000001010;
0B : 00000000000000000000000000001011;
0C : 00000000000000000000000000001100;
0D : 00000000000000000000000000001101;
0E : 10000000000000000000000000000000;
0F : 01111111111111111111111111111111;

END;
```

Figure 2: SRAM Memory Initialization File

## LPM AddSub 32 bits

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  -- Top-level entity
4  ENTITY addersubtractor2 IS
5  |   GENERIC (n : INTEGER := 32);
6  |   PORT (
7  |       A, B : IN STD_LOGIC_VECTOR(n - 1 DOWNTO 0);
8  |       Clock, Reset, Sel, AddSub, Aload, Bload, Zload : IN STD_LOGIC;
9  |       Z, Aout, Bout : BUFFER STD_LOGIC_VECTOR(n - 1 DOWNTO 0);
10 |       Overflow : OUT STD_LOGIC
11 |   );
12 | END addersubtractor2;
13 | ARCHITECTURE Behavior OF addersubtractor2 IS
14 |   SIGNAL G, M, Areg, Breg, Zreg : STD_LOGIC_VECTOR(n - 1 DOWNTO 0);
15 |   SIGNAL SelR, AddSubR, over_flow : STD_LOGIC;
16 |   COMPONENT mux2to1
17 |     GENERIC (k : INTEGER := 32);
18 |     PORT (
19 |       V, W : IN STD_LOGIC_VECTOR(k - 1 DOWNTO 0);
20 |       Selm : IN STD_LOGIC;
21 |       F : OUT STD_LOGIC_VECTOR(k - 1 DOWNTO 0)
22 |     );
23 |   END COMPONENT;
24 |   COMPONENT megaddsub
25 |     PORT (
26 |       add_sub : IN STD_LOGIC;
27 |       dataa, datab : IN STD_LOGIC_VECTOR(31 DOWNTO 0);
28 |       result : OUT STD_LOGIC_VECTOR(31 DOWNTO 0);
29 |       overflow : OUT STD_LOGIC
30 |     );
31 |   END COMPONENT;
```

Figure 3: LPM AddSub 32 bits Part I

```
32 BEGIN
33 -- Define flip-flops and registers
34 PROCESS (Reset, Clock)
35 BEGIN
36 IF Reset = '1' THEN
37   Areg <= (OTHERS => '0');
38   Breg <= (OTHERS => '0');
39   Zreg <= (OTHERS => '0');
40   SelR <= '0';
41   AddSubR <= '0';
42   Overflow <= '0';
43 ELSIF Clock'EVENT AND Clock = '1' THEN
44   SelR <= Sel;
45   AddSubR <= NOT AddSub;
46   Overflow <= over_flow;
47   IF Aload = '1' THEN
48     Areg <= A;
49   END IF;
50   IF Bload = '1' THEN
51     Breg <= B;
52   END IF;
53   IF Zload = '1' THEN
54     Zreg <= M;
55   END IF;
56 END IF;
57 END PROCESS;
58 -- Define combinational circuit
59 nbit_addsub : megaddsub
60 PORT MAP(AddSubR, G, Breg, M, over_flow);
61 multiplexer :
62   mux2to1
63   GENERIC MAP(k => n)
64   PORT MAP(Areg, Z, SelR, G);
65   Z <= Zreg;
66   Aout <= Areg;
67   Bout <= Breg;
68 END Behavior;
```

Figure 4: LPM AddSub 32 bits Part II

```
69 -- k-bit 2-to-1 multiplexer
70 LIBRARY ieee;
71 USE ieee.std_logic_1164.ALL;
72 ENTITY mux2to1 IS
73   GENERIC (k : INTEGER := 32);
74   PORT (
75     V, W : IN STD_LOGIC_VECTOR(k - 1 DOWNT0 0);
76     Selm : IN STD_LOGIC;
77     F : OUT STD_LOGIC_VECTOR(k - 1 DOWNT0 0)
78   );
79 END mux2to1;
80 ARCHITECTURE Behavior OF mux2to1 IS
81 BEGIN
82   PROCESS (V, W, Selm)
83   BEGIN
84     IF Selm = '0' THEN
85       F <= V;
86     ELSE
87       F <= W;
88     END IF;
89   END PROCESS;
90 END Behavior;
```

Figure 5: LPM AddSub 32 bits Part III

```

93  LIBRARY ieee;
94  USE ieee.std_logic_1164.ALL;
95  LIBRARY lpm;
96  USE lpm.lpm_components.ALL;
97  ENTITY megaddsub IS
98  PORT (
99      add_sub : IN STD_LOGIC;
100     dataa : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
101     datab : IN
102         STD_LOGIC_VECTOR (31 DOWNTO 0);
103     result : OUT
104         STD_LOGIC_VECTOR (31 DOWNTO 0);
105     overflow : OUT
106         STD_LOGIC
107 );
108 END megaddsub;
109 ARCHITECTURE SYN OF megaddsub IS
110     SIGNAL sub_wire0 : STD_LOGIC;
111     SIGNAL sub_wire1 : STD_LOGIC_VECTOR (31 DOWNTO 0);
112     COMPONENT lpm_add_sub
113     GENERIC (
114         lpm_width : NATURAL;
115         lpm_direction : STRING;
116         lpm_type : STRING;
117         lpm_hint :
118             STRING
119 );

```

Figure 6: LPM AddSub 32 bits Part IV

```

120     PORT (
121         dataa : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
122         add_sub : IN STD_LOGIC;
123         datab : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
124         overflow : OUT STD_LOGIC;
125         result : OUT STD_LOGIC_VECTOR (31 DOWNTO 0)
126 );
127 END
128 COMPONENT;
129 BEGIN
130     overflow <= sub_wire0;
131     result <= sub_wire1(31 DOWNTO 0);
132     lpm_add_sub_component :
133     lpm_add_sub
134     GENERIC MAP(
135         lpm_width => 32,
136         lpm_direction => "UNUSED",
137         lpm_type => "LPM_ADD_SUB",
138         lpm_hint => "ONE_INPUT_IS_CONSTANT=NO,CIN_USED=NO")
139     PORT MAP(
140         dataa => dataa,
141         add_sub => add_sub,
142         datab => datab,
143         overflow => sub_wire0,
144         result => sub_wire1
145 );
146 END SYN;

```

Figure 7: LPM AddSub 32 bits Part V

The 32 bits add/subtractor is able to add 32 bits number reading from given data A, and data B and perform operation based on the signal “AddSub”, addition if “AddSub” = 0, and subtraction if “AddSub” = 1, this will perform operation when signal “Zload” is called to load the new value to Z based on the “AddSub” signal. Signal “Aload” and “Bload” are used to load value to A and B from the input “SRAM” by using demux to

select which number the SRAM will input into this 32 bit Add/Subtractor. The overflow signal is used to alert the user if an overflow occurs.

## Demux 1 to 2

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  entity demux1to2 is
5      generic (n : INTEGER := 32);
6      port ( i : in std_logic_vector(n-1 downto 0);
7            sel : in std_logic;
8            o1 : out std_logic_vector(n-1 downto 0);
9            o2 : out std_logic_vector(n-1 downto 0));
10 end demux1to2;
11
12 architecture demux1to2_arch of demux1to2 is
13 begin
14     process (i, sel)
15     begin
16         case sel is
17             when '0' =>
18                 o1 <= i;
19                 o2 <= (others => '0');
20             when '1' =>
21                 o1 <= (others => '0');
22                 o2 <= i;
23             when others =>
24                 o1 <= (others => '0');
25                 o2 <= (others => '0');
26         end case;
27     end process;
28 end demux1to2_arch;

```

Figure 8: Demultiplexer 1 to 2

The Demux is used to connect the SRAM to the add/subtractor for reading the value from the SRAM based on a given address.

## Test Bench

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity addersubtractor2_tb is
6  end addersubtractor2_tb;
7
8  architecture addersubtractor2_tb_arch of addersubtractor2_tb is
9
10     component sram is
11     port
12     (
13         address : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
14         clock    : IN STD_LOGIC := '1';
15         data     : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
16         wren     : IN STD_LOGIC;
17         q        : OUT STD_LOGIC_VECTOR (31 DOWNTO 0)
18     );
19     end component;
20
21     component addersubtractor2 is
22     generic (n : INTEGER := 32);
23     port (
24         A, B : IN STD_LOGIC_VECTOR(n - 1 DOWNTO 0);
25         Clock, Reset, Sel, AddSub, Aload, Bload, Zload : IN STD_LOGIC;
26         Z, Aout, Bout : BUFFER STD_LOGIC_VECTOR(n - 1 DOWNTO 0);
27         Overflow : OUT STD_LOGIC
28     );
29     end component;

```

Figure 9: Test Bench Part I

```

31 component demux1to2 is
32     generic (n : INTEGER := 32);
33     port (i : in std_logic_vector(n-1 downto 0);
34           sel : in std_logic;
35           o1 : out std_logic_vector(n-1 downto 0);
36           o2 : out std_logic_vector(n-1 downto 0));
37     end component;
38
39
40 signal address: std_logic_vector(3 downto 0) := "0000";
41 signal clock, reg_sel, Reset, Sel, Aload, Bload, Zload, AddSub, Overflow: std_logic := '0';
42 signal data_in, data_out, A, B, Z, Aout, Bout: std_logic_vector(31 downto 0);
43

```

Figure 10: Test Bench Part II



```
begin
    sram_inst: sram
    port map (
        address => address,
        clock => clock,
        data => data_in,
        wren => '0',
        q => data_out
    );

    demux_inst: demux1to2
    port map(
        i => data_out,
        sel => reg_sel,
        o1 => A,
        o2 => B
    );

    addersubtractor2_inst: addersubtractor2
    port map(
        A => A,
        B => B,
        Clock => clock,
        Reset => Reset,
        Sel => Sel,
        AddSub => AddSub,
        Aload => Aload, Bload => Bload, Zload => Zload,
        Z => Z,
        Aout => Aout,
        Bout => Bout,
        Overflow => Overflow
    );

    process
    begin
        clock <= '0';
        wait for 5 ns;
        clock <= '1';
        wait for 5 ns;
    end process;
```

*Figure 11: Test Bench Part III*

This Test bench will perform every operation every 5 ns. This testbench file is used to connect all the necessary components together in order to perform addition and subtraction using value within the SRAM.

## Addition of Two Integers X1 + X2 VHDL

```
88 process
89 begin
90     -- Test Case 1 x1 + x2
91     -- 100 ns Total
92     Aload <= '1';
93     address <= "1010"; -- address 10
94     wait for 20 ns;
95
96     wait for 10 ns;
97     Aload <= '0';
98     wait for 10 ns;
99     reg_sel <= '1';
100    address <= "0010"; -- address 2
101    wait for 20 ns;
102    Bload <= '1';
103    wait for 20 ns;
104    Bload <= '0';
105
106    Zload <= '1';
107    wait for 10 ns;
108    Zload <= '0';
109    reg_sel <= '0';
110    wait for 10 ns;
111
112    -- Test Case 1 Ended
113    -- Reset for next Test case
114    Reset <= '1';
115    wait for 10 ns;
116    Reset <= '0';
117    wait for 10 ns;
```

Figure 12: Add X1 + X2

## Subtraction of Two Integers X1 - X2 VHDL

```
119 -- Test Case 2 x1 - x2
120 -- 110 ns
121 AddSub <= '1';
122 wait for 10 ns;
123 Aload <= '1';
124 address <= "1100"; -- address 12
125 wait for 20 ns;
126
127 wait for 10 ns;
128 Aload <= '0';
129 wait for 10 ns;
130 reg_sel <= '1';
131 address <= "0110"; -- address 6
132 wait for 20 ns;
133 Bload <= '1';
134 wait for 20 ns;
135 Bload <= '0';
136
137 Zload <= '1';
138 wait for 10 ns;
139 Zload <= '0';
140 reg_sel <= '0';
141 AddSub <= '0';
142 wait for 10 ns;
143
144 -- Test Case 2 Ended
145 -- Reset for next Test Case
146 Reset <= '1';
147 wait for 10 ns;
148 Reset <= '0';
149 wait for 10 ns;
```

Figure 13: Sub X1 - X2

**Cumulative Sum  $X1 + X2 + X3 + X4$  VHDL**

```

151 -- Test Case 3 x1 + x2 + x3 + x4
152 -- 200 ns
153 Aload <= '1';
154 address <= "0001"; -- address 1
155 wait for 20 ns;
156
157 wait for 10 ns;
158 Aload <= '0';
159 wait for 10 ns;
160 reg_sel <= '1';
161 address <= "0010"; -- address 2
162 wait for 20 ns;
163 Bload <= '1';
164 wait for 20 ns;
165 Bload <= '0';
166 zload <= '1';
167 Sel <= '1';
168 wait for 10 ns;
169
170 zload <= '0';
171 address <= "0011"; -- Load data from address 3
172 wait for 20 ns;
173 Bload <= '1';
174 wait for 20 ns;
175 Bload <= '0';
176 Zload <= '1';
177 wait for 10 ns;
178 zload <= '0';
179 address <= "0100"; -- Load data from address 4
180 wait for 20 ns;
181 Bload <= '1';
182 wait for 20 ns;
183 Bload <= '0';
184 zload <= '1';
185 wait for 10 ns;
186 zload <= '0';
187 reg_sel <= '0';
188 Sel <= '0';
189 wait for 10 ns;
190
191 -- Test Case 3 Ended
192 -- Reset for next Test Case
193 Reset <= '1';
194 wait for 10 ns;
195 Reset <= '0';
196 wait for 10 ns;

```

*Figure 14: Add  $X1 + X2 + X3 + X4$*

**Cumulative Subtract X1 - X2 - X3 - X4 VHDL**

```

198 -- Test Case 4 x1 - x2 - x3 - x4
199 -- 210 ns
200 AddSub <= '1';
201 wait for 10 ns;
202 Aload <= '1';
203 address <= "1101"; -- Load data from address 13
204 wait for 20 ns;
205
206 wait for 10 ns;
207 Aload <= '0';
208 wait for 10 ns;
209 reg_sel <= '1';
210 address <= "0011"; -- Load data from address 3
211 wait for 20 ns;
212 Bload <= '1';
213 wait for 20 ns;
214 Bload <= '0';
215 zload <= '1';
216 Sel <= '1';
217 wait for 10 ns;
218 zload <= '0';
219 address <= "0010"; -- Load data from address 2
220 wait for 20 ns;
221 Bload <= '1';
222 wait for 20 ns;
223 Bload <= '0';
224 zload <= '1';
225 wait for 10 ns;
226 zload <= '0';
227 address <= "0001"; -- Load data from address 1
228 wait for 20 ns;
229 Bload <= '1';
230 wait for 20 ns;
231 Bload <= '0';
232 zload <= '1';
233 wait for 10 ns;
234 zload <= '0';
235 reg_sel <= '0';
236 AddSub <= '0';
237 Sel <= '0';
238 wait for 10 ns;
239
240 -- Reset for next Test Case
241 Reset <= '1';
242 wait for 10 ns;
243 Reset <= '0';
244 wait for 10 ns;

```


*Figure 15: Sub X1 - X2 - X3 - X4*

**Overflow VHDL**

```

246      -- Test Case 5 Overflow
247      Aload <= '1';
248      address <= "1111"; -- address 16
249      wait for 20 ns;
250
251      wait for 10 ns;
252      Aload <= '0';
253      wait for 10 ns;
254      reg_sel <= '1';
255      address <= "0001"; -- address 1
256      wait for 20 ns;
257      Bload <= '1';
258      wait for 20 ns;
259      Bload <= '0';
260
261      Zload <= '1';
262      wait for 10 ns;
263      Zload <= '0';
264      reg_sel <= '0';
265      wait for 10 ns;
266
267      end process;

```

 *Figure 16: Overflow***III. Simulation****Addition of Two Integers  $X1 + X2$** *Figure 17: Add  $X1 + X2$  Simulation*

As you can see we first load from address 0000000A into A which is the value 10 in decimal, after we which turn the signal “reg\_sel” to load the second value from address

Meng Wai Chan

May 13, 2023

00000002 into B. then we perform the adding operation by loading their sum into Z.

which is  $10 + 2 = 12$ .

### Subtraction of Two Integers X1 - X2

 


Figure 18: Sub X1 - X2 Simulation

This simulation is similar to the Addition as we load the number to A and B, then perform the operation by calling the “Zload” signal, to output the final value into Z.

### Cumulative Sum X1 + X2 + X3 + X4

 


Figure 19: Add X1 + X2 + X3 + X4 Simulation

May 13, 2023

This simulation is performing  $1 + 2 + 3 + 4$ . Which respectively are 00000001, 00000002, 00000003, 00000004, addresses from the MIF file, the result 10 is outputted into Z.

### Cumulative Subtract X1 - X2 - X3 - X4

 


Figure 20: Sub  $X1 - X2 - X3 - X4$  Simulation

This simulation is performing 13 - 3 - 2 - 1. Which respectively are 00000000C, 000000003, 000000002, 000000001, addresses from the MIF file, the result 10 is outputted into Z.



## Overflow

 


Figure 21: Overflow Simulation

The overflow demonstration is adding the largest possible integer + 1, which is  $7FFFFFFF + 00000001$  which is  $80000000$ , and the overflow signal is turned into 1.

## IV. Conclusion

In this lab, we used SRAM as a memory to store data at a specified address. The SRAM is connected to a demultiplexer which directs the data to either input A or input B of an adder-subtractor based on the value of the 'reg\_sel' signal. The adder-subtractor uses a MegaAddSub component and a multiplexer to allow for selecting either the output Z or input A values using the 'Sel' signal. By setting the 'Sel' signal, we can select Z, which allows for cumulative addition and subtraction. We tested the circuit using basic arithmetic operations such as addition and subtraction of two numbers, as well as cumulative addition and subtraction. Additionally, we tested the 'Overflow' signal by adding a number to the most positive number, which triggers the 'Overflow' signal to indicate that the result is out of range and cannot be represented using the given number of bits.